



Thévenin's theorem

Oriol Gomis & Eduardo Prieto


CITCEA-UPC

oriol.gomis@upc.edu // eduardo.prieto-araujo@upc.edu

Thévenin's Theorem

Basics


- Thévenin's theorem is one of the most important theorems of electric circuits
- The theorem was independently derived in 1853 by Hermann von Helmholtz and in 1883 by Léon Charles Thévenin
- *Any linear electrical network with voltage and current sources and impedances can be reduced to a two-terminal circuit consisting of a single voltage source in series with a single impedance*
- Thévenin's theorem allows to reduce complicated circuits to a single voltage source \underline{U}_{th} and a single impedance \underline{Z}_{th}

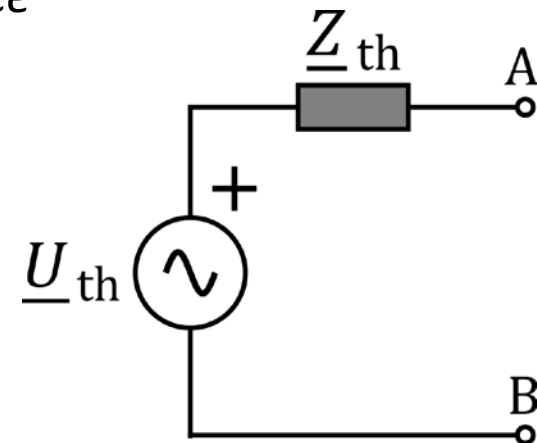

Thévenin's Theorem

Procedure to obtain a circuit Thévenin equivalent

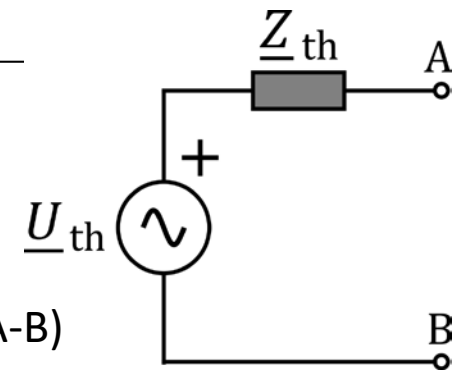
1. **Remove the load** from the circuit and label the two terminals (A-B)
2. **Determine the open circuit voltage** between the terminals A-B. The resulting open circuit voltage will be the value of the Thévenin voltage, \underline{U}_{th}
3. **Determine the Thévenin equivalent impedance** \underline{Z}_{th} by calculating the impedance “seen” between terminals A-B. Two different methods:
 1. Direct calculation of the impedance (no dependent sources and magnetic couplings in the circuit) using series-parallel association imposing:
 - Voltage sources are set to zero by replacing them with short circuits
 - Current sources are set to zero by replacing them with open circuits
 2. Short circuit current method
 - Short circuit terminals A-B, measure the short circuit current and calculate the Thévenin equivalent impedance \underline{Z}_{th} using the Thévenin voltage \underline{U}_{th}
4. **Draw and solve the equivalent circuit** using the calculated Thévenin voltage (Step 2) and the Thévenin impedance (Step 3), connecting the load



Thévenin's Theorem


Application example 1 – DC circuit

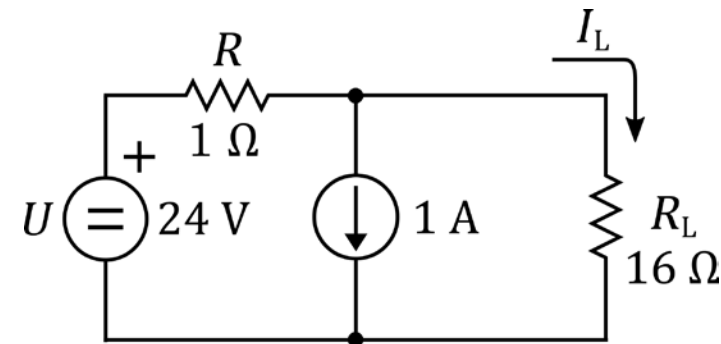- The same procedure is applied considering that impedances are resistances
- Objectives:
 - Obtain the Thévenin equivalent seen from the load R_L
 - Solve the circuit (obtain the load current I_L)



Procedure to obtain a circuit Thévenin equivalent (Example in DC current)

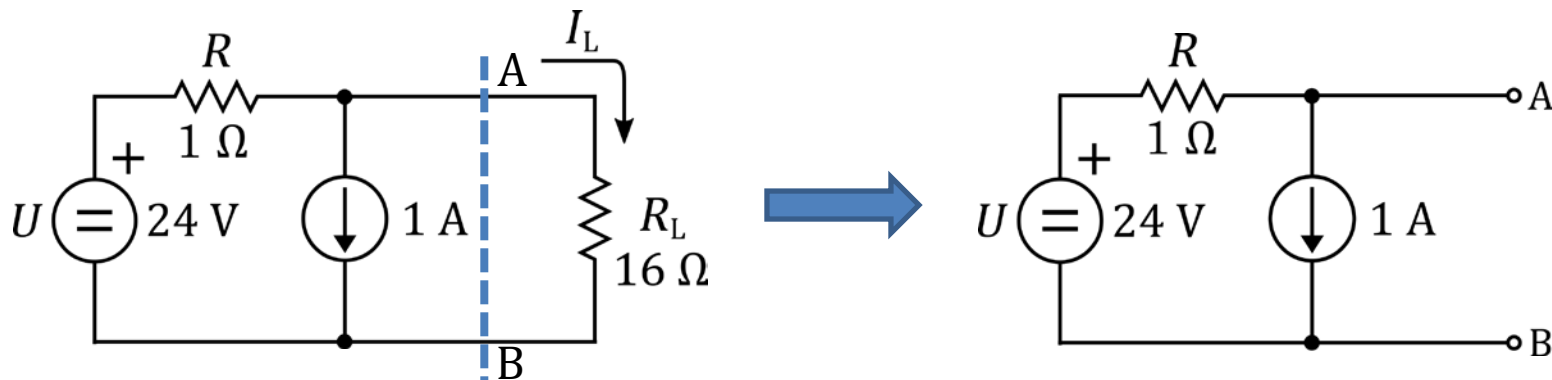
1. **Remove the load** from the circuit and label the two resulting terminals



Thévenin's Theorem

Procedure to obtain a circuit Thévenin equivalent (Example in DC current)

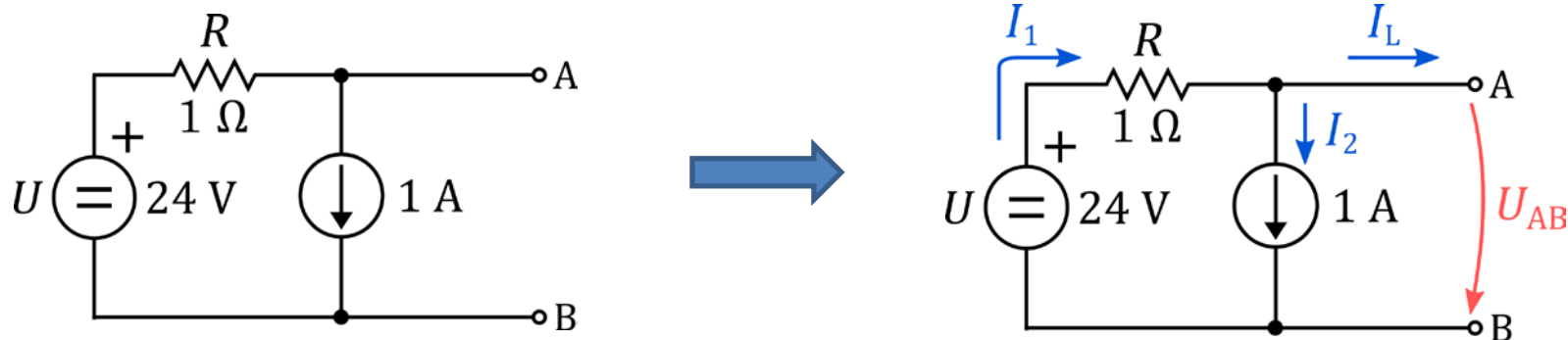- Determine the open circuit voltage** between the A-B terminals. The resulting open circuit voltage will be the value of the Thévenin voltage, U_{th} .



Circuit equations:

$$\left. \begin{aligned} I_1 &= I_2 + \cancel{I_L} = I \\ U - U_{AB} &= R I \end{aligned} \right\} \quad U_{th} = U_{AB} = U - R I = 24 - 1 \cdot 1 = 23 \text{ V}$$


Thévenin's Theorem

Procedure to obtain a circuit Thévenin equivalent (Example in DC current)

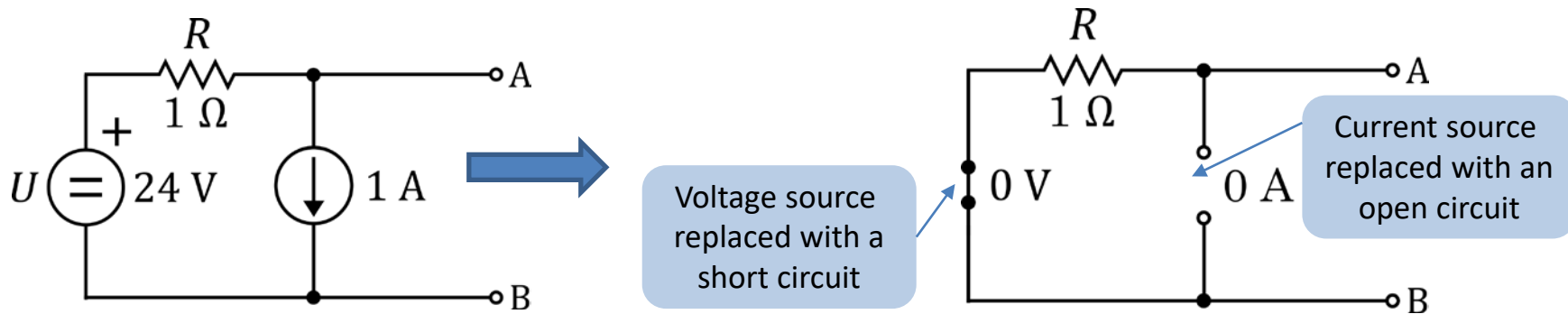
3. **Determine the Thévenin equivalent resistance R_{th}** by calculating the resistance “seen” between terminals A-B

‘**Direct calculation method**’ is used for this example (simple DC circuit)

- Set the voltage and current sources to zero



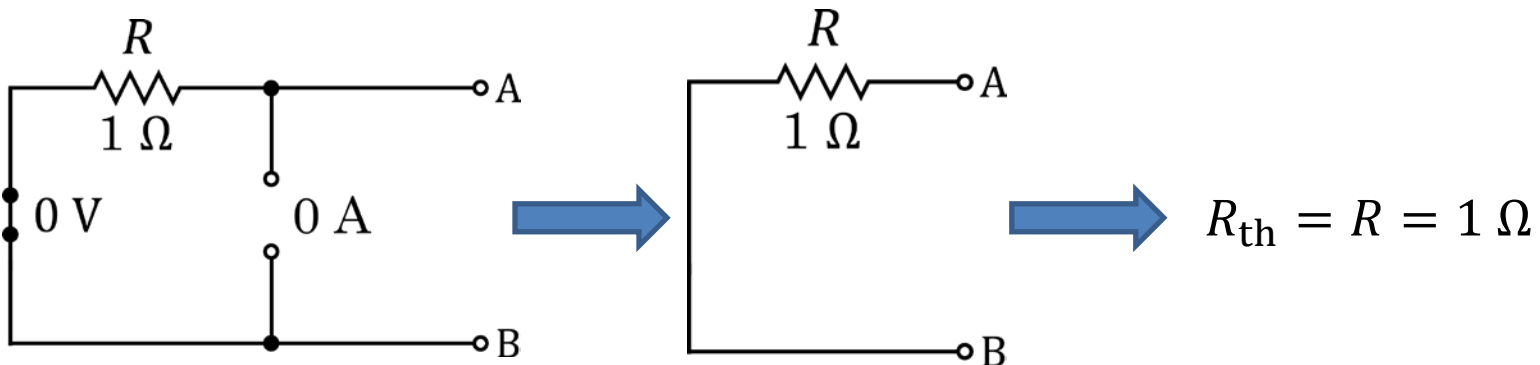
- Calculate the equivalent ‘seen’ from A-B



Thévenin's Theorem

Procedure to obtain a circuit Thévenin equivalent (Example in DC current)

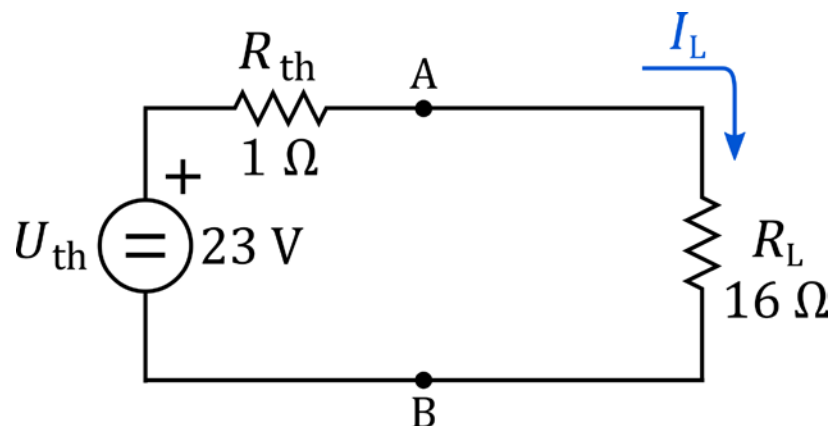4. **Draw the equivalent circuit** using the calculated Thévenin voltage (Step 2) and the Thévenin resistance (Step 3), connecting again the load



Then, the **circuit can be solved**


$$U_{th} = (R_{th} + R_L) I_L \quad \longrightarrow \quad I_L = \frac{U_{th}}{R_{th} + R_L} \quad \longrightarrow \quad I_L = \frac{23}{1 + 16} = 1,35 \text{ A}$$

The positive sign of the current means that it is following in the same direction as we have assumed

Thévenin's Theorem

Understanding the results


The original circuit is:

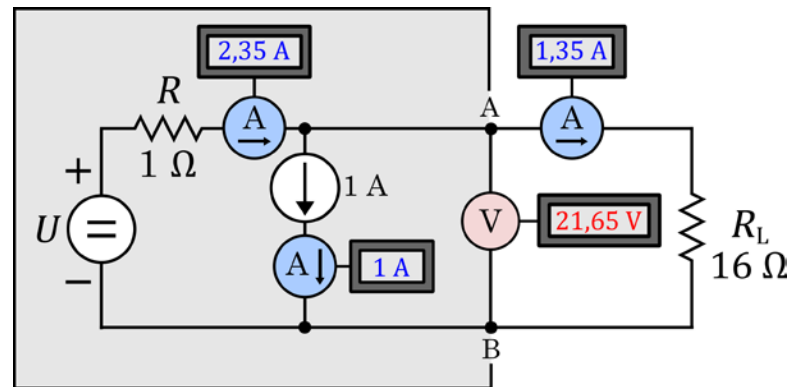

And its Thévenin equivalent circuit:

$$U_{th} = 23\text{ V}$$

$$R_{th} = 1\ \Omega$$

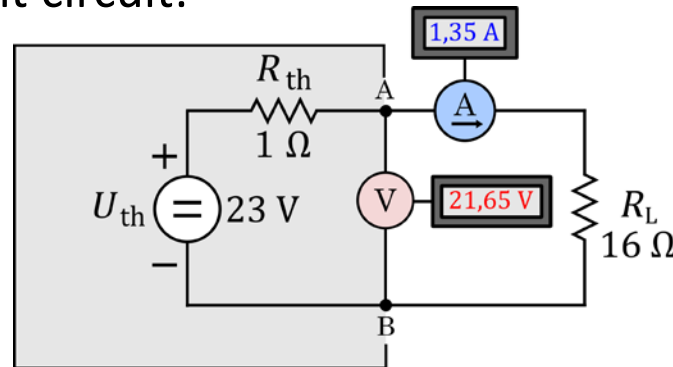


In both circuits the same voltage is applied to the load and therefore the current is identical

Thévenin's Theorem


Application example 2 – AC circuit

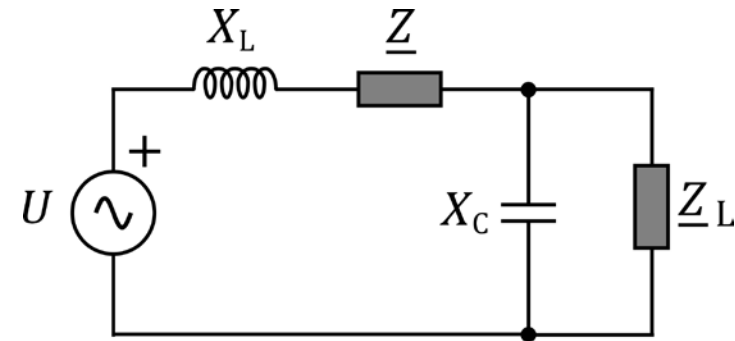- Objective: obtain the Thévenin equivalent seen from the load \underline{Z}_L and solve the circuit
- Circuit data:
 - Voltage: 230 V
 - Frequency: 50 Hz
 - Load: $\underline{Z}_L = 50 + j2 \Omega$
 - $X_L = 0,5 \Omega$
 - $X_C = 200 \Omega$
 - $\underline{Z} = 2 + j2 \Omega$



Procedure to obtain a circuit Thévenin equivalent (Example in AC current)

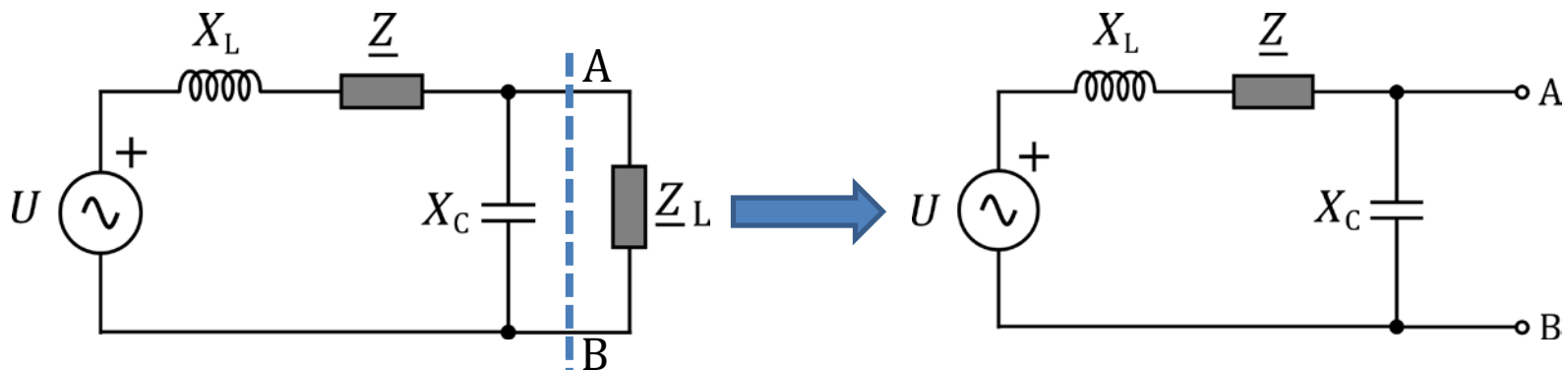
- Remove the load** from the circuit and label the two resulting terminals



Thévenin's Theorem

Procedure to obtain a circuit Thévenin equivalent (Example in AC current)

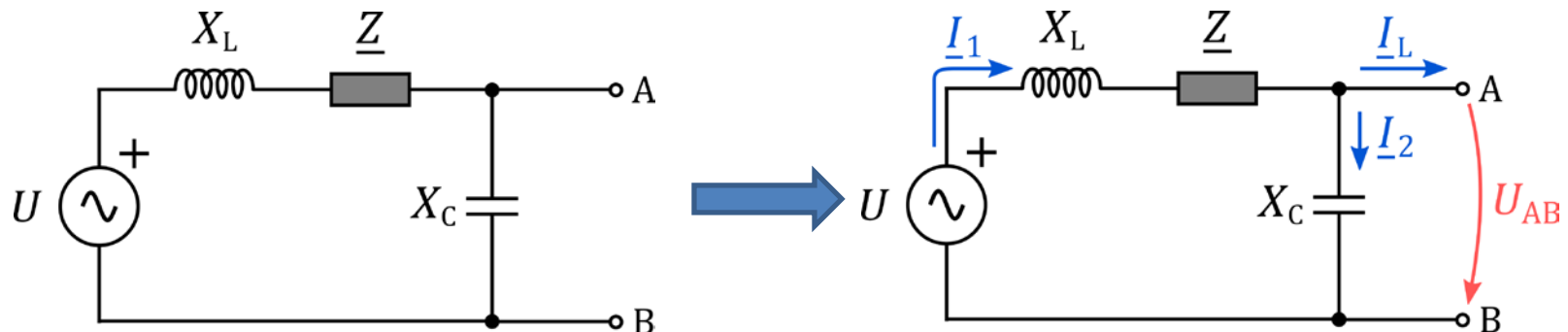- Determine the open circuit voltage** between the A-B terminals. The resulting open circuit voltage will be the value of the Thévenin voltage, \underline{U}_{th} .



Circuit equations:

$$\left. \begin{aligned} \underline{I}_1 &= \underline{I}_2 + \cancel{\underline{I}_L} = \underline{I} \\ \underline{U} &= \underline{I} (jX_L + \underline{Z} - jX_C) \\ \underline{U}_{AB} &= -jX_C \underline{I} \\ \underline{U} &= U \end{aligned} \right\} \quad \underline{I} = \frac{U}{jX_L + \underline{Z} - jX_C} = \frac{230}{j0,5 + (2 + j2) - j200} = 0,012 + j1,16 \text{ A}$$

$$\underline{U}_{th} = \underline{U}_{AB} = -jX_C \underline{I} = 232,89 - j2,35 \text{ V}$$

$$U_{th} = 232,90 \text{ V}$$


Thévenin's Theorem

Procedure to obtain a circuit Thévenin equivalent (Example in AC current)


3. **Determine the Thévenin equivalent impedance \underline{Z}_{th}** by calculating the impedance “seen” between terminals A-B.

First, the ‘**Direct calculation method**’ is used.

- Set the voltage source to zero

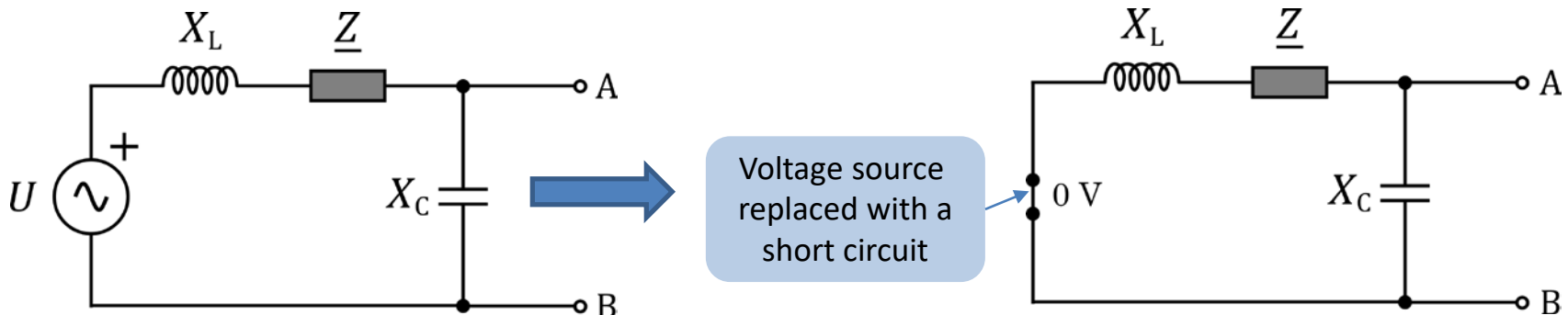

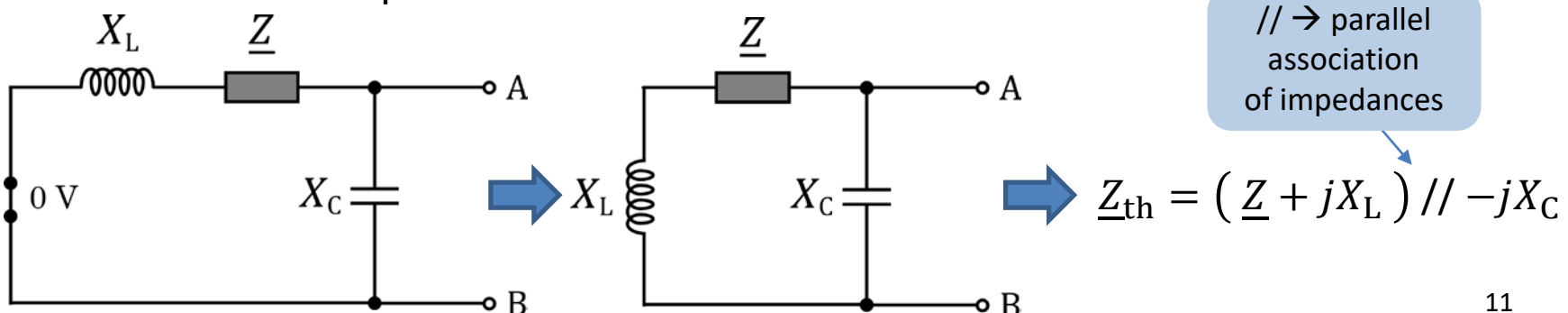
- Calculate the equivalent ‘seen’ from A-B



Thévenin's Theorem

Procedure to obtain a circuit Thévenin equivalent (Example in AC current)

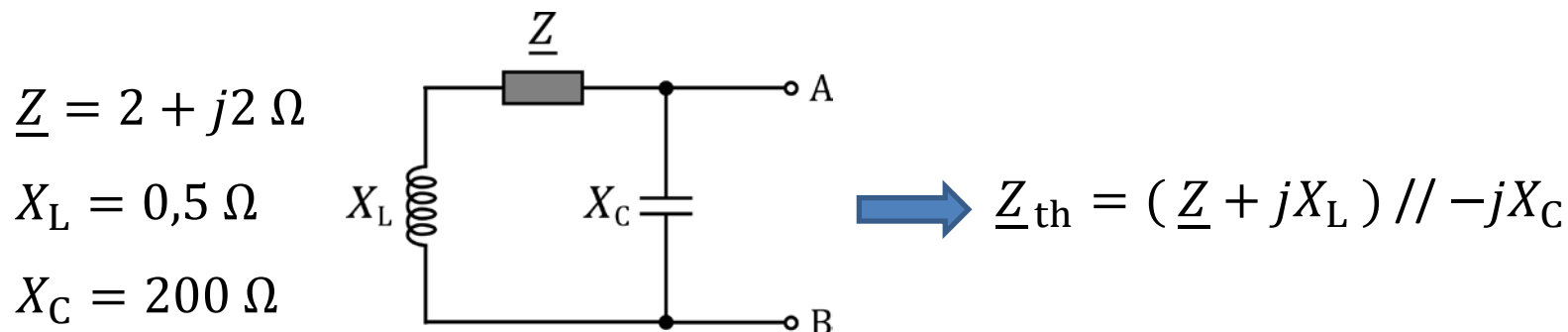3. Based on the **'Direct calculation method'**, the impedance can be calculated using the following data:



$$\underline{Z}_{th} = \frac{1}{\frac{1}{jX_L + \underline{Z}} + \frac{1}{-jX_C}} = \frac{1}{\frac{1}{j0,5 + (2 + j2)} + \frac{1}{-j200}} = 2,05 + j2,51 \Omega$$


This method is limited to simple circuits that can be reduced by series-parallel associations. It is not applicable if magnetic couplings are present in the circuit.

Thévenin's Theorem

Procedure to obtain a circuit Thévenin equivalent (Example in AC current)

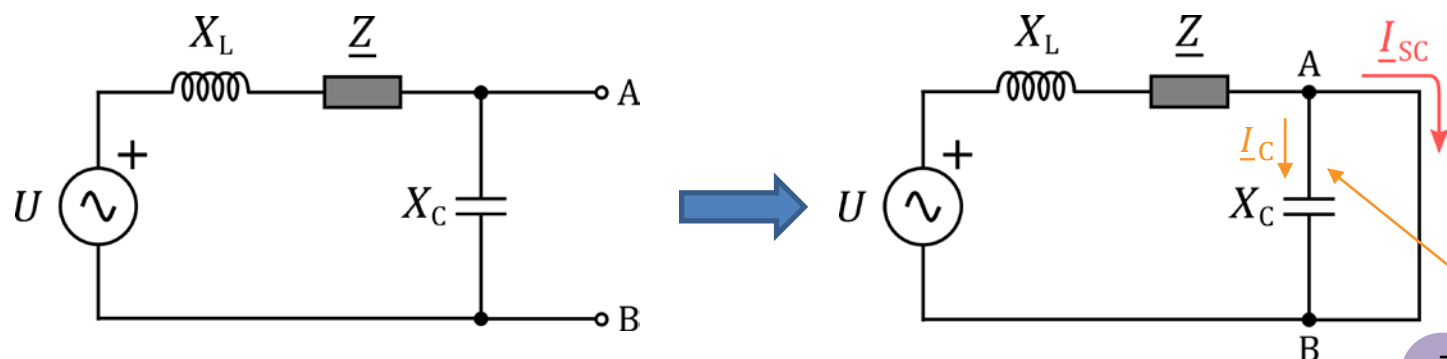3. An alternative method to find the Thévenin impedance is the '**Short-circuit current method**' which does not have limitations as the 'Direct impedance method'. It can be applied as follows

- Create a short circuit between A and B in the initial circuit



- And calculate the short circuit current


$$\left. \begin{array}{l} \underline{U} = (jX_L + \underline{Z}) \underline{I}_{sc} \\ \underline{U} = U \end{array} \right\} \underline{I}_{sc} = \frac{U}{(jX_L + \underline{Z})} = \frac{230}{(j0,5 + 2 + j2)} = 44,88 - j56,10 \text{ A}$$

The current through this branch will be 0 due to the short circuit

Thévenin's Theorem

Procedure to obtain a circuit Thévenin equivalent (Example in AC current)

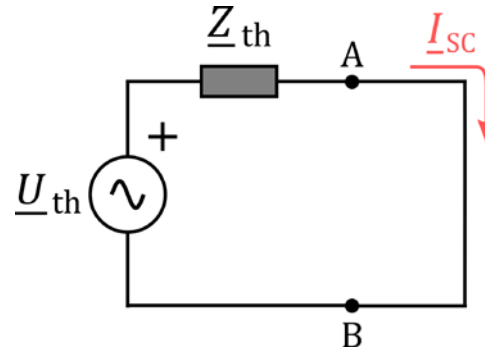3. Similarly, applying a short-circuit to the Thévenin equivalent



- The Thévenin impedance can be expressed as

$$\underline{U}_{th} = \underline{Z}_{th} \underline{I}_{sc} \longrightarrow \underline{Z}_{th} = \frac{\underline{U}_{th}}{\underline{I}_{sc}}$$

- Then, based on the obtained Thévenin voltage and short circuit current, the Thévenin impedance is:


$$\underline{Z}_{th} = \frac{\underline{U}_{th}}{\underline{I}_{sc}} = \frac{232,89 - j2,35}{44,88 - j56,09} = 2,05 + j2,51 \, \Omega$$

- Impedance comparison between methods
 - Direct method: $\underline{Z}_{th} = 2,05 + j2,51 \, \Omega$
 - Short circuit method: $\underline{Z}_{th} = 2,05 + j2,51 \, \Omega$

Thévenin's Theorem

Procedure to obtain a circuit Thévenin equivalent (Example in AC current)

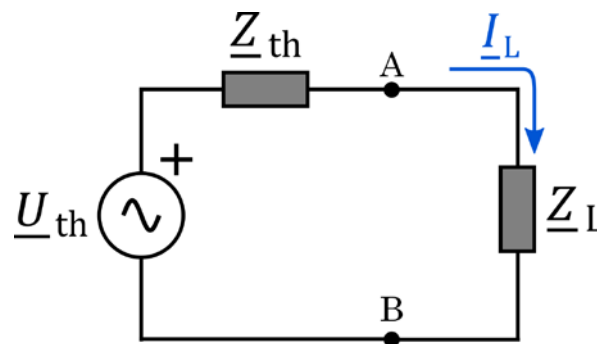4. **Draw the equivalent circuit** using the calculated Thévenin voltage (step 2) and the Thévenin impedance (Step 3), connecting again the load.



Then, the **circuit can be solved**

$$\underline{U}_{th} = (\underline{Z}_{th} + \underline{Z}_L) \underline{I}_L \rightarrow \underline{I}_L = \frac{\underline{U}_{th}}{(\underline{Z}_{th} + \underline{Z}_L)} = 4,44 - j0,43 \text{ A}$$


Then, the current flowing through the circuit is

$$I_L = 4,46 \text{ A}$$


Thévenin's Theorem

Understanding the results

The original circuit is:

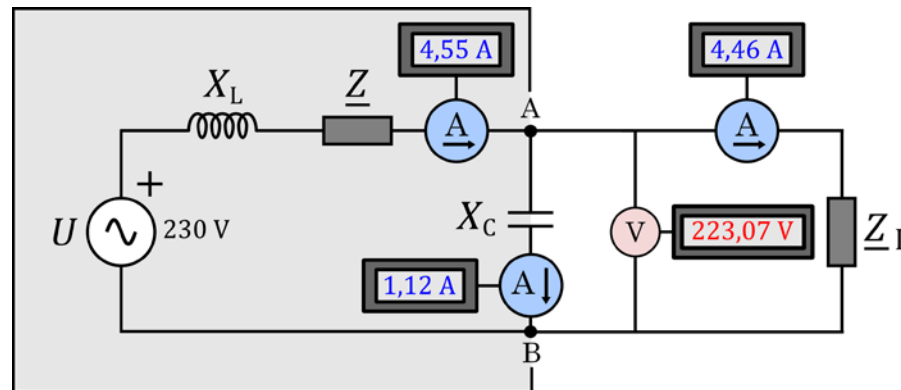


And its Thévenin equivalent circuit:

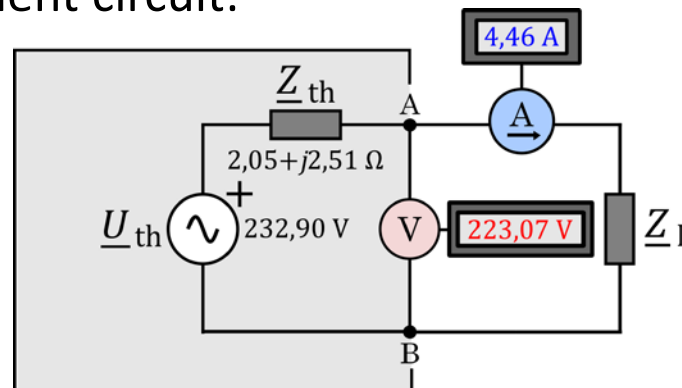

$$\underline{U}_{th} = 232,89 - j2,35 \text{ V}$$

$$\underline{Z}_{th} = 2,05 + j2,51 \Omega$$

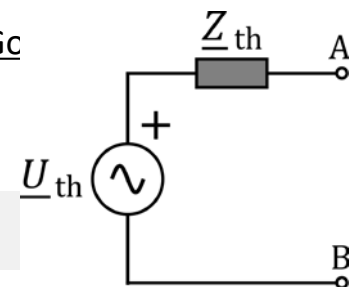In both circuits the same voltage is applied to the load and therefore the current is identical.



Grid Thévenin equivalent

Short circuit power

- Usually, electric companies use the Thévenin equivalent to characterize a certain point of the network. Two concepts should be previously defined (according to IEC*):
 - The **Short circuit power** S_{SC} is the **product between the current in the short circuit** at a point of a system, and a **conventional voltage**, generally the operating voltage.
 - The **grid operating voltage** U_g in a system is the value of the **voltage under normal conditions**, at a given instant and a given point of the system (this value may be expected, estimated or measured)
- Then, the grid Thévenin equivalent can be calculated as

$$U_{th} = U_g \quad Z_{th} = \frac{U_g^2}{S_{SC}}$$


- The ratio between R and X of the grid impedance Z_{th} depends on the type of grid (transmission or distribution)

*IEC (International Electrotechnical Commission)

Relevant Thévenin application case

Thévenin circuit equivalent connected to a load

- The problem to be solved is:

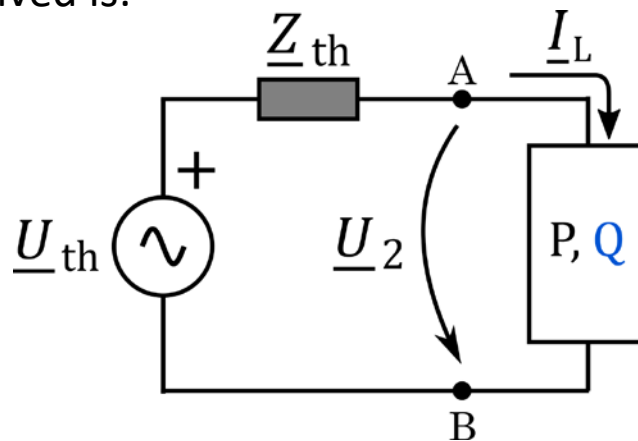


- It is a simple 'Power flow analysis' case, considering only two nodes.
- Two different cases can be differentiated based on the known data
 - It is assumed that the Grid Thévenin is known (\underline{U}_{th} and \underline{Z}_{th})
 - Case 1: P and Q known – Find voltage \underline{U}_2
 - Case 2: P and \underline{U}_2 known – Find reactive power Q

Relevant Thévenin application case

Case 1: P and Q known, U_2 unknown

- The problem to be solved is:

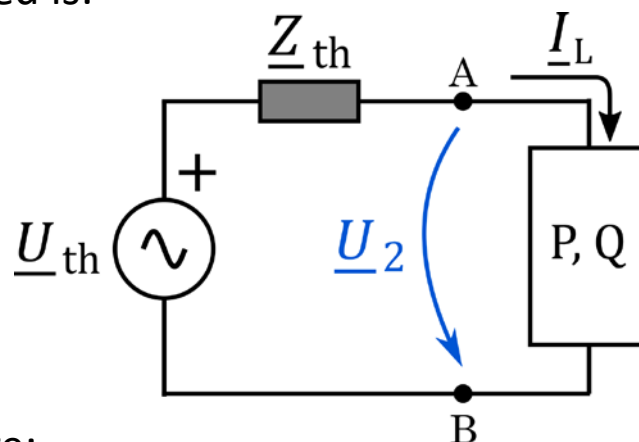

- The circuit equations are:

$$\text{Equation 1: } \underline{U}_{th} = \underline{Z}_{th} \underline{I}_L + \underline{U}_2 = (R_{th} + jX_{th}) \underline{I}_L + \underline{U}_2$$

$$\text{Equation 2: } \underline{S} = \underline{U}_2 \underline{I}_L^* = P + jQ \longrightarrow \underline{I}_L^* = \frac{\underline{S}}{\underline{U}_2} \longrightarrow \underline{I}_L = \frac{\underline{S}^*}{\underline{U}_2^*}$$

- Substituting the expression of the current \underline{I}_L in equation 1

$$\underline{U}_{th} = (R_{th} + jX_{th}) \frac{\underline{S}^*}{\underline{U}_2^*} + \underline{U}_2 \xrightarrow{\times \underline{U}_2^*} \underline{U}_{th} \underline{U}_2^* = (R_{th} + jX_{th}) \underline{S}^* + \overbrace{\underline{U}_2 \underline{U}_2^*}^{U_2^2}$$

Relevant Thévenin application case

Case 1: P and Q known, U_2 unknown

- Then:

$$\underline{U}_{th} \underline{U}_2^* = (R_{th} + jX_{th})\underline{S}^* + U_2^2$$

$$\underline{U}_{th} \underline{U}_2^* = (R_{th} + jX_{th})(P - jQ) + U_2^2$$

- Operating the previous equation:


$$\underline{U}_{th} \underline{U}_2^* = R_{th}P - jR_{th}Q + jX_{th}P - j^2X_{th}Q + U_2^2$$

$$\underline{U}_{th} \underline{U}_2^* = \underbrace{R_{th}P + X_{th}Q + U_2^2}_{\text{Real part}} + j\underbrace{(X_{th}P - R_{th}Q)}_{\text{Imaginary part}}$$

- Then, calculating the square of the absolute value of the previous expression

$$U_{th}^2 U_2^2 = \underbrace{(R_{th}P + X_{th}Q + U_2^2)^2}_{\text{Real part}} + \underbrace{(X_{th}P - R_{th}Q)^2}_{\text{Imaginary part}}$$
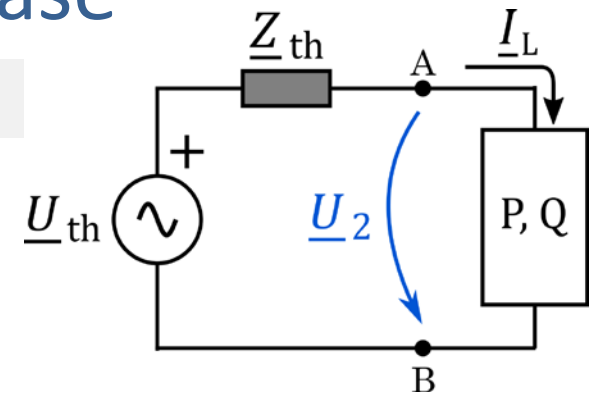
$$U_{th}^2 U_2^2 = R_{th}^2 P^2 + X_{th}^2 Q^2 + U_2^4 + 2R_{th}P X_{th}Q + 2R_{th}P U_2^2 + 2X_{th}Q U_2^2 + \\ + X_{th}^2 P^2 + R_{th}^2 Q^2 - 2R_{th}P X_{th}Q$$



Relevant Thévenin application case

Case 1: P and Q known, U_2 unknown

- Reordering the previous expression

$$U_2^4 - U_{th}^2 U_2^2 + R_{th}^2 P^2 + X_{th}^2 Q^2 + 2R_{th}P U_2^2 + 2X_{th}Q U_2^2 + X_{th}^2 P^2 + R_{th}^2 Q^2 = 0$$

- Knowing that:

$$R_{th}^2 P^2 + X_{th}^2 Q^2 + X_{th}^2 P^2 + R_{th}^2 Q^2 = \overbrace{(R_{th}^2 + X_{th}^2)}^{Z_{th}^2} \overbrace{(P^2 + Q^2)}^{S^2} = Z_{th}^2 S^2$$

- The expression can be simplified as

$$U_2^4 - U_{th}^2 U_2^2 + 2R_{th}P U_2^2 + 2X_{th}Q U_2^2 + Z_{th}^2 S^2 = 0$$

- Simplifying (U_2^2 common factor):

$$U_2^4 - U_2^2 (U_{th}^2 - 2(R_{th}P + X_{th}Q)) + Z_{th}^2 S^2 = 0$$

- Provided that

$$\text{Re}(\underline{Z}_{th} \underline{S}^*) = \text{Re}((R_{th} + jX_{th})(P - jQ)) = \overbrace{\text{Re}(R_{th}P - j^2 X_{th}Q - jR_{th}Q + jX_{th}P)}^{R_{th}P + X_{th}Q}$$

- Then, the final expression to obtain the load voltage U_2 is:

$$U_2^4 - U_2^2 (U_{th}^2 - 2 \text{Re}(\underline{Z}_{th} \underline{S}^*)) + Z_{th}^2 S^2 = 0$$

Relevant Thévenin application case

Case 1: P and Q known, U_2 unknown

- Then, the equation must be solved

$$U_2^4 - U_2^2(U_{th}^2 - 2 \operatorname{Re}(\underline{Z}_{th} \underline{S}^*)) + Z_{th}^2 S^2 = 0$$

- As an example:

- Voltage: $\underline{U}_{th} = 230 \text{ V}$

- Frequency: 50 Hz

- Impedance: $\underline{Z}_{th} = 0,5 + j1,2 \Omega$


- Load:

- $P = 1 \text{ kW}$

- $\cos \varphi = 0,9$

$$S = \frac{P}{\cos \varphi}$$


- The numeric solutions of the biquadratic equation are $\pm 225,16 \text{ V}$ and $\pm 6,42 \text{ V}$
- Considering the positive values: $225,16 \text{ V}$ and $6,42 \text{ V}$
- Finally, the adequate solution should be selected, considering the system operational voltage and its constraints. The most suitable solution is $U_2 = 225,16 \text{ V}$ as the voltage magnitude is close to the grid 230 V value

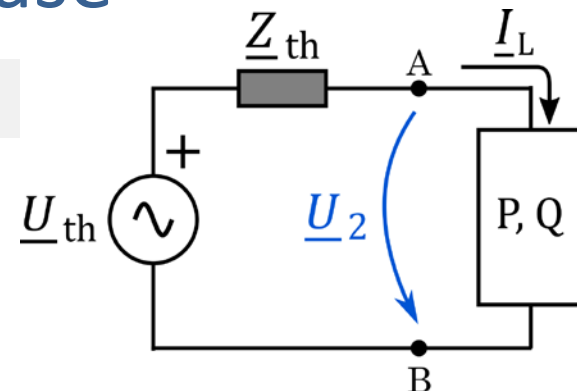

Relevant Thévenin application case

Case 1: P and Q known, U_2 unknown

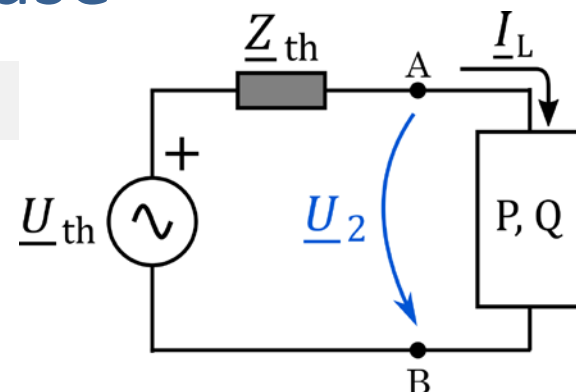- In order to confirm this selection, the current flowing through the circuit can be obtained (taking U_2 as reference)



$$\underline{S} = U_2 \underline{I}_L^* = P + jQ \longrightarrow \underline{I}_L = \frac{\underline{S}^*}{U_2}$$


- The current for both solutions are
 - For $U_2 = 225,16 \text{ V} \rightarrow I_L = 4,93 \text{ A}$ (logical current)
 - For $U_2 = 6,42 \text{ V} \rightarrow I_L = 173,20 \text{ A}$ (high current)
- Also, the equivalent impedance of the load can be obtained:

$$\left. \begin{array}{l} \underline{S} = U_2 \underline{I}_L^* \\ \underline{U}_2 = \underline{Z}_L \underline{I}_L \end{array} \right\} \underline{Z}_L = \frac{U_2^2}{\underline{S}^*} \longrightarrow \underline{Z}_L = 41,06 + j19,89 \Omega$$

Relevant Thévenin application case

Understanding the results


The obtained results can be depicted as

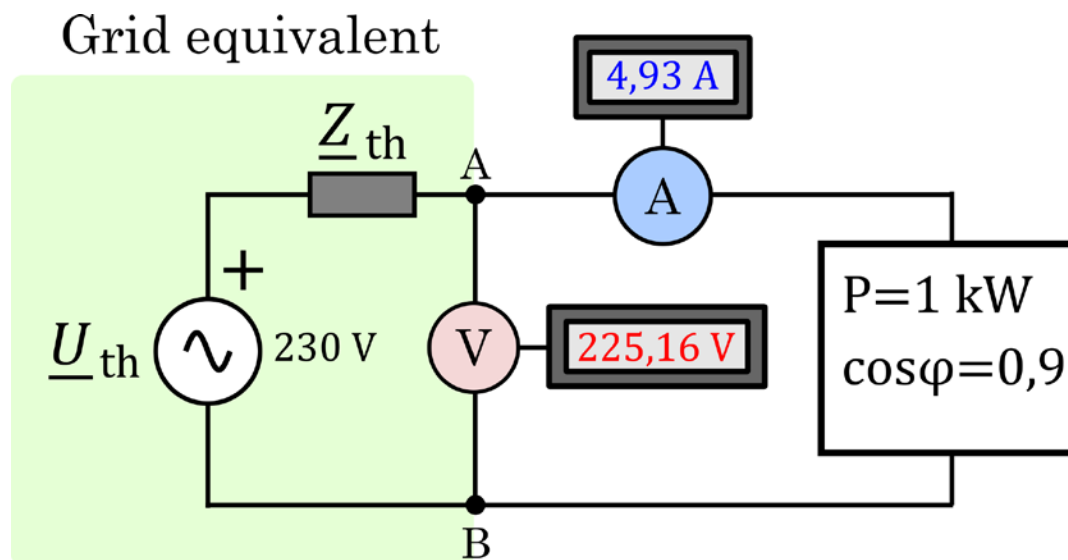

Relevant Thévenin application cases

Case 2: P and U_2 known, Q unknown

- The problem to be solved is:

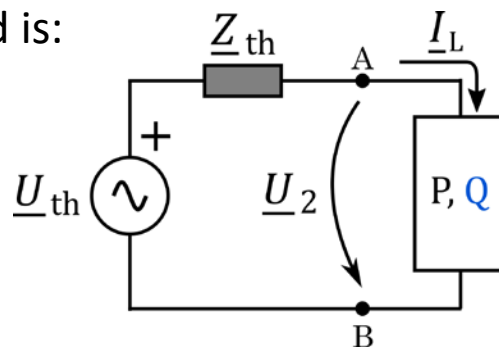

- Recalling the obtained expression:

$$U_2^4 - U_2^2 \left(U_{th}^2 - 2\text{Re}(\underline{Z}_{th} \underline{S}^*) \right) + Z_{th}^2 \underline{S}^2 = 0$$

- Expanding terms

$$U_2^4 - U_{th}^2 U_2^2 + 2R_{th}P U_2^2 + 2X_{th}Q U_2^2 + Z_{th}^2 (P^2 + Q^2) = 0$$

$$U_2^4 - U_{th}^2 U_2^2 + 2R_{th}P U_2^2 + 2X_{th}Q U_2^2 + Z_{th}^2 P^2 + Z_{th}^2 Q^2 = 0$$

- Then, the reactive power can be obtained:

$$Q^2 Z_{th}^2 + 2X_{th} U_2^2 Q + (U_2^4 - U_{th}^2 U_2^2 + 2R_{th}P U_2^2 + Z_{th}^2 P^2) = 0$$